

# Application Note AN-65

## LYTSwitch-5 Family

### Design Guide and Considerations

#### Introduction

The LYTSwitch™-5 family is ideal for single-stage power factor corrected constant current LED drivers for tubes, bulbs and recessed lighting up to 25 W. Each device combines a high-voltage power MOSFET, variable frequency and on-time control engine, fast start-up with soft-finish and protection functions including instantaneous line overvoltage shutdown, output short-circuit auto-restart, output overvoltage latch-off and thermal foldback with over-temperature shutdown into a single package, thus greatly reducing component count. Its internal feedback controller is capable of indirect and direct output current sensing that can be set via external programming resistor, thus eliminating the need for optocoupler, especially with isolated design applications.

The integrated 725 V power MOSFET provides a large drain voltage margin in high-line input AC applications, thus increasing reliability. A 625 V power MOSFET option is also offered to reduce cost in applications where the voltage stress on the power MOSFET is low.

Topology neutral LYTSwitch-5 operates in discontinuous conduction mode (DCM) for tight tolerance output current regulation over line input range and operating temperature, high power factor with significantly low harmonic currents via its internal control algorithm. The combination of a low-side switching topology, cooling via electronically quiet SOURCE pins, frequency jitter and DCM operation which inherently eliminates reverse current from the output diode when the power MOSFET is in OFF-state reducing high frequency noise. This allows the use of a simple and small input pi filter yet produces low EMI (note that low input capacitance reduces THD and increases PF).

#### Typical Circuit Configuration

The LYTSwitch-5 device family is topology neutral that it can be used in any switching configuration such as Buck (Tapped-Buck), Buck-Boost (Tapped Buck-Boost), Boost and Flyback (Isolated and Non-Isolated) making it broadly applicable to any design requirement regardless of LED voltage string. The high level integration of LYTSwitch-5 family enables ease of design optimization both in converter and EMI sections resulting to shortened development time.

Circuit in Figures 1 and 2 show a typical low component count universal LED driver using LYTSwitch-5 in Buck and isolated Flyback configurations respectively.

 


Figure 1. Low Component Count Typical Circuit Buck Topology with LYTSwitch-5 (21 external components).

 


Figure 2. Low Component Count Typical Circuit Isolated Flyback Topology with LYTSwitch-5 (23 external components).

#### Output Power Table

Product	Output Power
	90-308 VAC
LYT5225D	9 W
LYT5216D, LYT5226D	16 W
LYT5218D, LYT5228D	25 W

Table 1. LYTSwitch-5 Output Power Table. See LYTSwitch-5 data sheet for more details.

**Scope**

This application note is intended for users designing an AC-DC LED driver using LYTSwitch-5 family devices. A simplified step by step instruction will guide the user in selecting key components, especially in designing the magnetics necessary to quickly jump start the design process and come up with a sound prototype design. This application note refers directly to the PIXIs design spreadsheet that is a part of the PI Expert™ design software suite (<https://piexpertonline.power.com/site/login>).

In this application note the user may also find product Reference Design Kits (RDK) and Design Example Reports (DER) useful. These contain a prototype board, a link to an engineering report that contains complete design information including gerber for the printed

circuit board (PCB) and test data and product samples. Further details on downloading PI Expert, RDKs and updates to this document can be found at Power Integrations' website [www.power.com](http://www.power.com).

**Choosing Switching Topology**

The LYTSwitch-5 device family can be used in any switching topology configuration such as Buck (Tapped-Buck), Buck-Boost (Tapped Buck-Boost), Boost and Flyback (Isolated and Non-Isolated) making it broadly applicable to any design requirement regardless of LED voltage string. Choosing the right topology to use can be challenging at times, however using LYTSwitch-5 the designer only needs to know is the output voltage, efficiency and ATHD target in choosing the suitable topology to use. Table 2 shows a topology selection guide.

Output Voltage (V)		Recommended Topology					Remark
Low-Line/ Universal Inputs	High-Line Inputs	Tapped Buck or Buck-Boost	Buck	Buck-Boost	Boost	Flyback	
< 12	< 25	✓					Limited by maximum duty of device at minimum input voltage
13 – 60	27 - 100		✓				Minimum voltage is limited by maximum on-time of device at maximum input
> 24	> 48			✓			Maximum output voltage is limited by transistor breakdown voltage
$V_{OUT} > V_{IN}$					✓		
Any Voltage > 3						✓	
Minimum Efficiency Estimate		>80%	>87%	>85%	>90%	80%	
ATHD%		>15%	>15%	5% < x < 15%	>25%	5% < x < 15%	

Table 2. Recommended Topology Selection Guide.

## Design Example

Design a 12 W non-isolated LED driver using LYTSwitch-5 having an output voltage of 75 V, output current of 160 mA,  $\pm 5\%$  regulation tolerance with an input voltage range of 90 VAC to 264 VAC, 89% minimum efficiency, and THD <15%.

## Step-by-Step Design Procedure

Referring to Table 2, a Buck-Boost topology can be suitable for this particular specification hence the corresponding PIXls designer spreadsheet will be used. All PIXls designer spreadsheets are available at Power Integrations website, <https://piexpertonline.power.com/site/login>

### Step 1: Enter Application Variables

**Enter: Minimum, Nominal and Maximum Input Voltages; VAC<sub>MIN</sub> [C3], VAC<sub>NOM</sub> [C4], VAC<sub>MAX</sub> [C5], F<sub>L</sub> [C6]**

2	ENTER APPLICATION VARIABLES				Design Title
3	VACMIN	90.0	90.0	Volts RMS	Minimum AC line voltage.
4	VACNOM	230.0	230.0	Volts RMS	Nominal AC line voltage.
5	VACMAX	265.0	265.0	Volts RMS	Maximum AC line voltage.
6	FL		50	Hertz	AC line frequency.
7	VO_MIN		67.5	Volts DC	Guaranteed minimum VO that maintains output regulation.
8	VO	75.0	75.0	Volts DC	Worst case normal operating output voltage.
9	VO_OVP_MIN		85.3	Volts DC	Minimum Voltage at which output voltage protection may be activated.
10	IO	160.0	160.0	m-Amperes	Average output current specification.
11	EFFICIENCY	0.89	0.89	Dimensionless	Total power supply efficiency.
12	Z		0.50	Dimensionless	Loss allocation factor.
13	PO		12.00	Watts	Output power.

Figure 3. Application Variables Section of the PIXls Design Spreadsheet.

LYTSwitch-5 is intended for wide input voltage applications. It can maintain high efficiency, high power factor, low THD and tight regulations over entire input range.

Use Table 3 as reference for the input range to a particular regional requirement.

Region	Nominal Input (VAC)	Minimum Input (VAC)	Maximum Input (VAC)	Nominal Frequency (Hz)
Japan / USA	100 / 115	85	132	50 / 60
Europe / Rest of World	230 / 240	195	264	50 / 60
Lighting in commercial buildings in USA, (208 VAC phase-to-phase)	208 / 277	177	308	60

Table 3. Standard Worldwide Input Line Voltage Ranges and Line Frequencies.

**Enter: Nominal Output Voltage, V<sub>O</sub> [C8], Output Current I<sub>O</sub> [C10], EFFICIENCY [C11], Loss Allocation Factor, Z [C12]**

In a high power factor single stage LED driver, the output will have significantly large low frequency ripple with twice the frequency of the input line, it is recommended to use a power meter when measuring the output power for accuracy. PO [E13] is calculated based on the integral product of VO [C8] and IO [C10], which is used to choose device size.

$$P_o = \int I_{O(t)} \times V_{O(t)} dt$$

LYTSwitch-5 has built-in Latching Output Overvoltage Protection, once the current exceeds the I<sub>oov</sub> threshold via the OC pin, the IC will trigger a latch to disable switching thus preventing the output from rising further. Recycling the AC supply is needed to reset this protection mode from latch-off state.

The output overvoltage is detected through the bias supply which is calculated as VO\_OVP\_MIN by the PIXls. The accuracy of overvoltage set point will be dependent on the mutual inductance (M) between bias and output winding, that is the better the coupling the more accurate it gets. Therefore it is recommended to wind the bias winding close to the main winding.

For direct output voltage sensing, NS/NB = 1. Or for PIXls calculation, enter VBIAS [C76] = VO [C8].

The minimum voltage at which output voltage protection may be activated is calculated on cell VO\_OVP\_MIN [E9].

$$V_{O(OVP)MIN} = (R_{OC} \times I_{Oov} + V_{OC}) \times N/NB$$

Where,

R<sub>OC</sub>: Feedback resistor connected to OC pin from the rectified bias supply. Typical resistance value is set using 100  $\mu$ A OC current (IOC) based on the nominal output voltage and output current.

$$R_{OC} = (V_{BIAS} - V_{OC}) / I_{OC}$$

I<sub>oov</sub>: Latching Overvoltage Current Threshold. Minimum limit at 127  $\mu$ A.

V<sub>oc</sub>: OC pin voltage. Typical value at 2.2 V.

N: Output winding turns.

N<sub>b</sub>: Bias winding turns.

I<sub>oc</sub>: 100  $\mu$ A; default used to set the output current.

### Minimum Output Voltage, VO\_MIN [E7]

This calculates the minimum output voltage at which tight regulation can be maintained.

### Efficiency [C11], $\eta$

Use efficiency estimate in Table 2. Once the actual unit is available enter the measured efficiency for fine tuning the output current.

$$\eta = \frac{P_o}{P_{IN}}$$

### Loss Allocation Factor, Z [E12]

Allocation factor is the ratio of output and total loss. It is used in the efficiency of the DC-DC section of the converter for calculating the input power and drain current as seen by LYTSwitch-5. Typical value is 0.5.

$$Z = \frac{\text{Secondary Loss}}{\text{Total Losses}}$$

Step 2: LYTSwitch-5 Design Variables

17	LYTSwitch-5 DESIGN VARIABLES				
18	BREAKDOWN VOLTAGE	725		725 Volts DC	Choose between 650V and 725V.
19	GENERIC DEVICE	Auto		LYT52X6D	Chosen LYTSwitch-5 generic device.
20	ACTUAL DEVICE			LYT5226D	Chosen LYTSwitch-5 device code.
21	ILIMITMIN			1.767 Amperes	Minimum device current limit.
22	ILIMITTYP			1.900 Amperes	Typical Current Limit.
23	ILIMITMAX			2.033 Amperes	Maximum Current Limit.
24	IP_MOSFET			1.520 Amperes	Worst case peak drain current of the MOSFET.
25	TON_MIN			1.192 u-seconds	Worst case minimum on-time of the MOSFET.
26	TON_MAX			3.138 u-seconds	Worst case maximum on-time of the MOSFET.
27	IAVG_MOSFET			0.141 Amperes	Worst case average drain current of the MOSFET.
28	IRMS_MOSFET			0.301 Amperes	Worst case maximum RMS current of the MOSFET.
29	KDP			1.118 Dimensionless	Ratio between off-time of the MOSFET and on-time of the secondary diode.
30	VDRAIN			490.7 Volts DC	Estimated worst case drain voltage of the MOSFET.

Figure 4. LYTSwitch-5 Design Variables Section of PIXIs Design Spreadsheet.

The ACTUAL DEVICE [E20] will be automatically selected based on the output power calculated and input voltage. In the BREAKDOWN VOLTAGE [E18] cell, a 725 V part is automatically chosen for high-line input, while 650 V for low-line input. However, the user can override the default selection dependent on the requirement and choose a 650 V part, if the actual measured stress voltage on the MOSFET is much less than 650 V and/or choose a device with smaller MOSFET, if temperature margin requirement is not critical.

The corresponding data sheet current limit specifications ( $I_{LIMIT(MIN)}$  [E21],  $I_{LIMIT(TYP)}$  [E22], and  $I_{LIMIT(MAX)}$  [E23]) of the selected device are displayed, which are needed for calculating other design magnetic parameters.

**MOSFET Peak Current, IP\_MOSFET [E24]**

To ensure DCM operation, the theoretical highest operating peak current should not exceed device minimum current limit of device.

**Minimum ON-Time, TON\_MIN [E25]**

The minimum on-time operation is based on the minimum output voltage VO\_MIN [E7] to ensure tight output current regulation.

**Maximum ON-Time, TON\_MAX [E26]**

The maximum operating on-time (TON\_MAX) is based on the maximum tolerance of output voltage (assumed to be 110%) to ensure tight output current regulation.

**Device MOSFET Average and RMS Currents, IAVG\_MOSFET [E27], IRMS\_MOSFET [E28]**

MOSFET average current (IAVG\_MOSFET) and RMS current (IRMS\_MOSFET) are given to estimate the conduction loss of device MOSFET.

**Ripple to Peak Current Ratio, KDP [E29]**

Ratio between off-time of MOSFET and on-time of the secondary diode (Figure 5), KDP greater than 1 is recommended to ensure discontinuous conduction mode of operation.

 


Figure 5. Inductor Current Illustration. KDP of > 1 Ensures Discontinuous Conduction Mode (DCM) of Operation.

**MOSFET Drain to Source Voltage Stress, VDRAIN [E30]**

Drain to Source voltage stress ( $V_{DRAIN}$ ) is calculated based on maximum input voltage and 120% of  $V_o$  to account for overvoltage condition.

Step 3: Device Programming Parameters

DEVICE PROGRAMMING PARAMETERS				
35	RDO		6 k-ohms	DO pin resistor.
36	RDS		6 k-ohms	Current sense programming resistor connected to the DS pin for the buck-boost converter.

Figure 6. Device Programming Parameters Input of the Design Spreadsheet.

**Data Output Resistor, RDO [E35]**

Default value of 6 kΩ.

**Topology Selection Resistor RDS [E36]**

Resistor RDS is assigned a default value per PIX's design spreadsheet. There are two ways of sensing the output current with LYTSwitch-5 to maintain good regulation, that is Indirect (PSR) and Direct (SSR). These are topology dependent and programmed through RDS resistor value. With topologies where the output ground reference is not common with the input ground reference of the IC controller such as Buck or Isolated Flyback indirect current sensing (PSR) is used, this will eliminate the need for a use of a complex optocoupler or a level shifter circuitry. The sensing is done via the RDC sensing resistor where the signal is fed into the DRIVER CURRENT SENSE (DS) pin of the IC through the RDS resistor. The signal is processed internally and the interpolated value is outputted to the FEEDBACK (FB) pin which is filtered by  $C_{FB}$  and  $R_{FB}$  (Figure 7).

The latter is used if the ground references are common between the input and output circuitry. With direct sensing (SSR), the  $R_{DS}$  resistor is just simply connected to the SOURCE pin and the FEEDBACK pin is used to sense directly the output current via  $R_{FB2}$  sense resistor connected in series with the load and a small low pass filter ( $R_{FB}$  and  $C_{FB}$ ) is needed for the feedback signal (Figure 7).

RDS (Ω)	Current Sensing	Topology
6 k	Indirect or Primary Sense Regulation (PSR)	Buck, Buck-Boost, Isolated Flyback
24 k	Direct or Secondary Sense Regulation (SSR)	Non-Isolated Flyback, Boost

Table 4. RDS Resistor Selection for Topology Current Sensing.


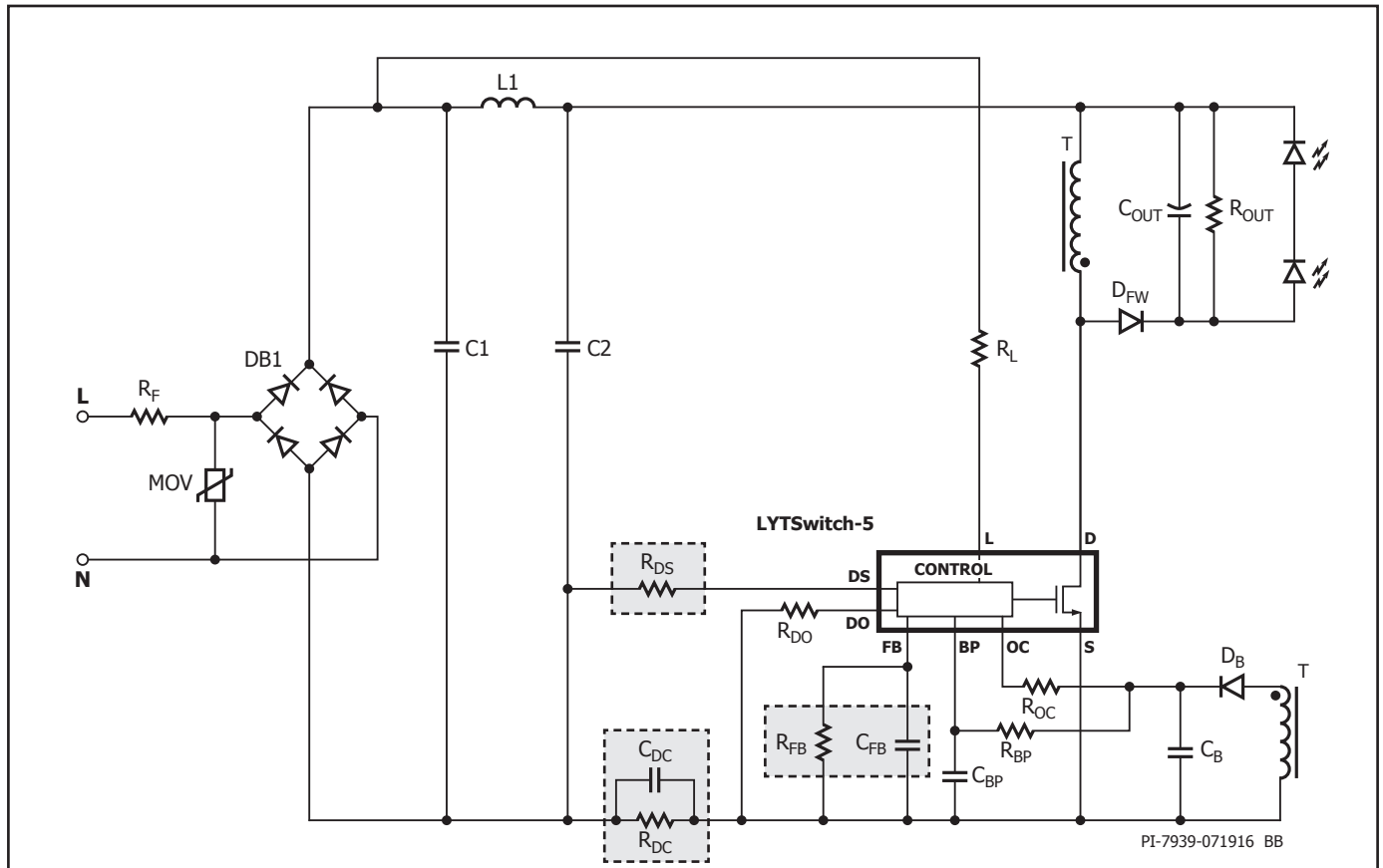


Figure 7. Schematic Shows  $R_{DS}$ ,  $R_{DC}$ ,  $R_{FB}$  and  $C_{FB}$  used for Indirect Sensing of Output Current with Buck-Boost Topology.

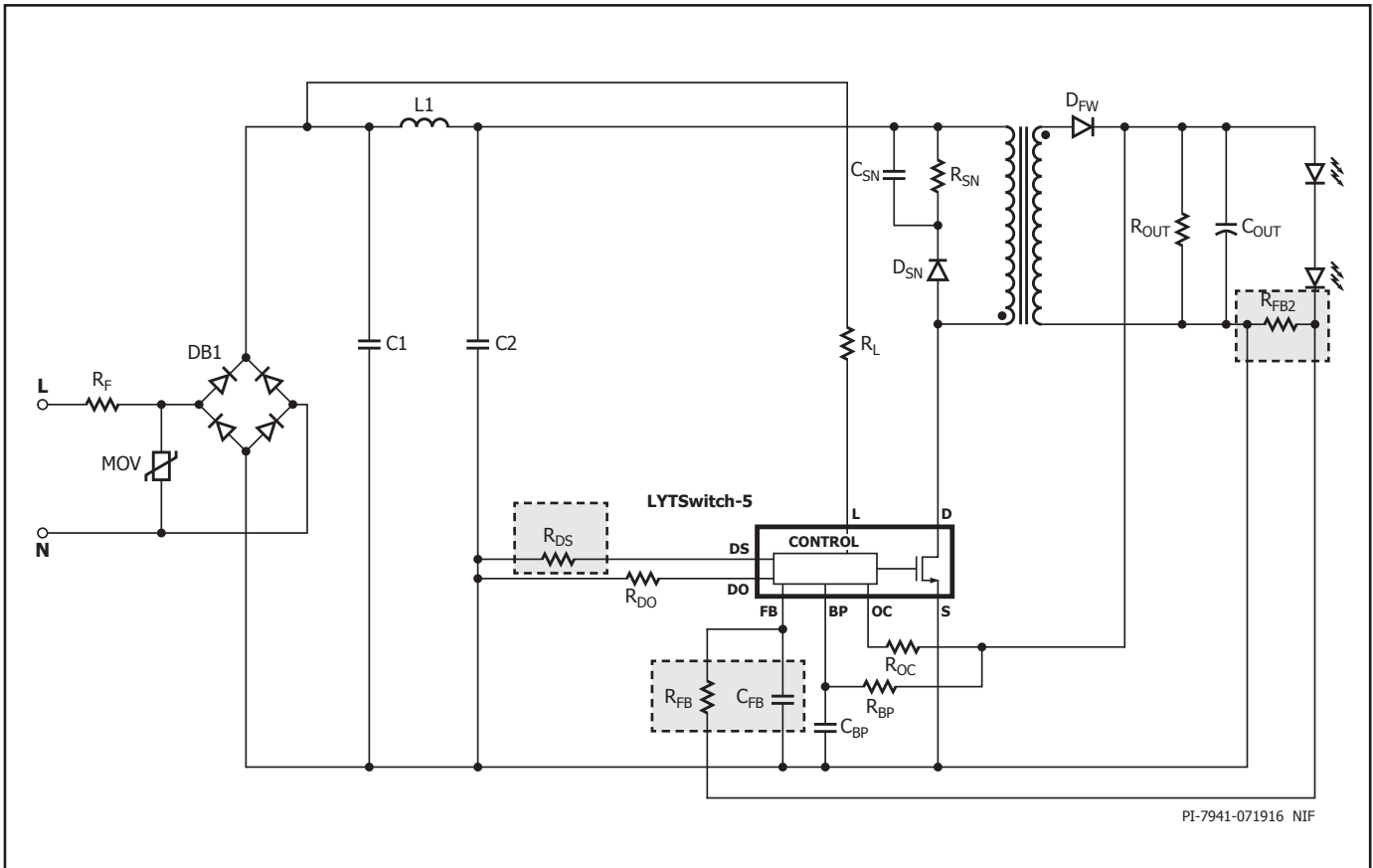

PI-7941-071916 NIF

Figure 8. Schematic Shows  $R_{DS}$ ,  $R_{FB2}$ ,  $R_{FB}$  and  $C_{FB}$  used for Direct Sensing of Output Current with Non-Isolated Flyback.

See schematic for other topologies in Appendix A.

**Step 4: Enter Inductor Core and Construction Variables**  
**CORE TYPE, AE, LE, AL, VE, AW, BW**

40	ENTER INDUCTOR CORE/CONSTRUCTION VARIABLES			
41	CORE TYPE	EFD15	EFD15	Core type.
42	AE		15.00 mm <sup>2</sup>	Core effective cross sectional area.
43	LE		34.00 mm	Core effective path length.
44	AL		700 nH/T <sup>2</sup>	Ungapped core effective inductance.
45	VE		510 mm <sup>3</sup>	Core volume.
46	AW		19.03 mm <sup>2</sup>	Window area of the bobbin.
47	BW		8.85 mm	Bobbin physical winding width.

Figure 9. Inductor Core and Construction Variables Input of the Design Spreadsheet.

Core type selection as a default is set in Auto. The spreadsheet will automatically choose the smallest, but commonly used core suitable for the output power specified. Should the designer prefers a different type of core to use, a list of common cores can be selected from the drop down menu in cell Core Type [C41] of the PIXIs spreadsheet or enter manually the parameters for the desired core to use.

Override cells can be used to enter the core and bobbin parameters onto cells AE [C42], LE [C43], AL [C44], VE [C45], AW [C46] and BW [C47]. This is useful if a preferred core is not on the list, or the specified core or bobbin information differs from that referenced by the spreadsheet.

## Step 5: Enter Transformer Design Parameters

TRANSFORMER DESIGN PARAMETERS					
51	TRANSFORMER DESIGN PARAMETERS				
52	Inductance parameters				
53	INDUCTANCE	325		325 u-Henrys	Typical value of inductance.
54	INDUCTOR_TOL	5		5 %	Tolerance of inductance.
55	INDUCTANCE_MIN			309 u-Henrys	Minimum value of inductance.
56	INDUCTANCE_MAX			341 u-Henrys	Maximum value of inductance.
57	N	121		121 Turns	Number of inductor turns.
58	ALG			22.20 nH/T <sup>2</sup>	Gapped core effective inductance.
59	BM			2857 Gauss	Maximum flux density.
60	BP			3822 Gauss	Peak flux density.
61	BAC			1429 Gauss	Worst case AC Flux Density for Core Loss Curves (0.5 X Peak to Peak).
62	LG			0.8 mm	Core gap length.
63	LAYERS_DESIRED			5 Dimensionless	Desired number of inductor's winding layers.
64	LAYERS_ACTUAL			4.61 Dimensionless	Actual number of inductor's winding layers.
65	AWG			29 AWG	Inductor's wire gauge.
66	OD_INDUCTOR_INSULATED			0.337 mm	Outer diameter of the inductor winding wire with insulation.
67	OD_INDUCTOR_BARE			0.286 mm	Outer diameter of the inductor winding wire without insulation.
68	IRMS_INDUCTOR			0.452 Amperes	Maximum RMS current flowing through the inductor's winding.
69	CMA_INDUCTOR			280 Cmil/A	Inductor winding CMA.
70	J_INDUCTOR			7.04 A/mm <sup>2</sup>	Inductor Winding Current density.
71	PRIMARY WINDING FILL FACTOR			72% Dimensionless	Percentage of bobbin window filled up by the inductor winding.

Figure 10. Transformer Design Parameters Section: Inductance Parameters of the Design Spreadsheet.

**Inductance [E53]**

This is the target nominal primary inductance for the main inductor. If left blank, the spreadsheet will calculate the inductance based on the VAC\_MIN [E53] to guarantee discontinuous conduction mode over the entire input range. User has the flexibility to override the calculation on cell [C53] and optimized the inductance according to desired operation.

**Inductor Tolerance [E54], Inductance\_Min [E55] and Inductance\_Max [E56]**

Expected inductance production tolerance can be assigned in cell [C54]. This tolerance is used in the calculation of the worst-case condition of electrical parameters for primary current and operating duty cycle.

**Inductor Turns, N [E57]**

This is the number of turns for the main primary-winding. The spreadsheet will automatically optimize the number of turns based on estimated Maximum Flux Density, BM [E59] and worst-case AC Flux Density BAC [E61]. User can assign number of turns on cell [C57] for necessary adjustment.

$$N = \text{INDUCTANCE}_{(MAX)} \times IP_{(MOSFET/BM)} \times A_E$$

**Gapped Core Effective Inductance, ALG [E58]**

ALG (nH/T<sup>2</sup>) is used in production of core to set the inductance of the transformer. It is used by the transformer vendor to specify the core center leg air gap. This is the value of inductance obtained for the squared number of turns around the core.

**Maximum Operating Flux Density, BM [E59]**

To avoid core saturation during normal operation at maximum operating temperature, a maximum value of 3300 Gauss is recommended.

**Peak Flux Density, BP [E60]**

A maximum 4200 Gauss is recommended to avoid core saturation. Peak flux density usually occurs during start-up and/or output

short-circuits conditions. The peak flux density is estimated at the maximum device current limit. It is important to verify that core saturation does not occur at maximum ambient temperature under start-up with maximum load.

$$BP = \text{INDUCTANCE}_{(MAX)} \times I_{LIMIT(MAX)/N} \times A_E$$

**AC Flux Density, BAC [E61]**

This is the flux density used in estimating the core loss for a given core material and volume in steady state condition.  $BAC = 0.5 \times BM$ .

**Core Gap Length, LG [E62]**

Gap used in the transformer production to set the correct inductance based on core material permeability (AL).

**Layers\_Desired [E63] and Layers\_Actual [E64]**

Number of winding layers used to estimate the size of magnetic wire to fit in the transformer bobbin.

**Transformer Wire Details, OD\_Diameter\_Insulated [E66]**

Outside wire diameter with insulation is calculated with the maximum diameter that allows the wire to fit given number of primary turns (N), bobbin width (BW) and assigned number of winding layers (L).

**Inductor RMS Current, IRMS\_Inductor [E68]**

The RMS current can be used to estimate winding copper loss of the inductor.

The other useful magnetic parameters given in the spreadsheet are: OD\_Inductor\_Bare [E67], diameter of wire without insulation. CMA\_Inductor [E69], inductor winding effective Circular Mils Area. Current\_Density [E70], inductor winding effective current density. Primary Winding Fill Factor [E71], percentage of bobbin window filled up by the primary winding to estimate if there is sufficient space.

Override cells [C53], [C54], [C57], [C63] and [C65] can be used to enter desired parameters.

**Step 6: Transformer Bias Winding and Bias Components**

Bias supply necessary to supply current into the BYPASS pin to operate normally even at all input and output conditions and also provides feedback information into the OC pin for regulation. The rectifier diode can be any fast or ultrafast recovery type with a voltage rating above the value given in the design spreadsheet (PIVBS [E77]), typically >200 V, and current rating >200 mA. The 1N4936 and UF4004 are good examples.

**Output Rectifier Maximum Peak Inverse Voltage, PIV<sub>BS</sub> [E77]**

This is maximum stress voltage across the bias diode at the maximum input voltage.

$$PIV_{BS} = BIAS_{TURNS/N} \times VAC_{MAX} \times \sqrt{2} + BIAS$$

Override cells [C74] and [C76] can be used to enter desired parameters for VD<sub>BIAS</sub> and V<sub>BIAS</sub> respectively.

73	Bias winding parameters				
74	VD_BIAS		0.70	Volts DC	Bias winding diode forward drop voltage.
75	BIAS_TURNS		21	Turns	Number of bias winding turns.
76	VBIAS		12.0	Volts DC	Bias Voltage. Check performance at minimum VO and VACMAX.
77	PIVBS		77.0	Volts DC	Output Rectifier Maximum Peak Inverse Voltage (calculated at VACMAX)
78	CBIAS		22.0	u-Farads	Bias winding rectification capacitor.
79	RBP		6.36	k-Ohms	Bias supply resistor assuming 1mA current necessary to supply the BP pin.
80	CBP		2.2	u-Farads	Minimum BP pin capacitance.

Figure 11. Transformer Bias Winding Parameters of the Design Spreadsheet.

**Bias Diode Forward Voltage Drop, VD\_BIAS [E74]**

Default value of typical forward voltage drop of 0.7 V for the bias rectifier diode.

**Bias Winding Turns, BIAS<sub>TURNS</sub> [E75]**

This is the number of turns of the bias winding calculated based on bias voltage chosen and output voltage.

$$BIAS_{TURNS} = (V_{BIAS} + VD_{BIAS}) / (V_O + VF_{DIODE}) \times N$$

**Bias Voltage, V<sub>BIAS</sub> [E76]**

Default value is 12 V the minimum value to ensure voltage supply for the bias to support the IC. Excessive voltage ripple is not recommended, at least 10 μF electrolytic capacitor filter must be used and if ceramic type capacitor is used, 22 μF value is recommended to account for huge tolerance for type of capacitor.

For designs which require a wider LED voltage operation, increasing the bias voltage to 20 V is recommended to maintain tight regulation with lower LED voltage.

**Step 7 Secondary Output Diode Parameters**

Use ultrafast diode for output rectification and the recommended diode rating should 2 times of the output current, i.e. 2x I<sub>o</sub> < I<sub>AVG(DIODE)</sub> for higher efficiency.

**Output Diode Voltage Drop, VF\_DIODE [E85]**

Enter the average forward voltage drop for the output diode. Use 0.7 V for a PN diode. Estimated forward power loss to this diode estimated by taking the product of I<sub>o</sub> × V<sub>F</sub>.

**Output Diode RMS Current, IRMS\_DIODE [E86]**

The RMS current through the diode is calculated that can be used to calculate the copper loss of the inductor.

**Output Diode Peak Current, IP\_DIODE [E87]**

Peak current in the output diode is calculated in a worst-case condition to guide the user to select the diode current rating and package size.

**Peak Inverse Diode Voltage, PIV\_DIODE [88]**

Use this parameter in selecting the voltage rating of the output diode. The worst-case reverse peak voltage is calculated in open load condition which is the worst-case condition.

For Buck-Boost;

$$PIV_{DIODE} = VAC_{MAX} \times \sqrt{2} + VO_{MAX}$$

84	SECONDARY DIODE PARAMETERS				
85	VF_DIODE		0.7	Volts DC	Output diode forward voltage drop.
86	IRMS_DIODE		0.375	Amperes	Diode RMS current at LP_MIN, VACMIN and PO_MAX
87	IP_DIODE		1.520	Amperes	Diode peak current at LP_MIN, VACMAX and PO_MAX
88	PIV_DIODE		506.0	Volts DC	Peak Inverse Voltage at VO_MAX on output diode.

Figure 12. Secondary Diode Parameters of the Design Spreadsheet.



## Step 8: Feedback and Protection Parameters with Fine Tuning

This section will guide the user in selecting the external parts to be used in the design for achieving the target output current. Leaving the section blank will recommend the initial value to be used in the prototype. Once the prototype has been built, the output current can be finely tuned using the override cells [C93], [C96], [C98], [C99] and [C101].

Low ESR ceramic type capacitor is recommended to use. Aluminum electrolytic capacitor due to its size, cost, relative high ESR and high capacitance tolerance is not recommended.

### Actual Bias Voltage, VBIAS\_MEASURED [E98]

Enter the actual bias voltage for fine tuning the output current. The actual may differ significantly from calculated due to leakage inductance of the transformer.

92	FEEDBACK AND PROTECTION PARAMETERS WITH FINE TUNING			
93	RL		3.74 M-Ohms	Standard (E96 / 1%) L pin resistor.
94	OVP_LINE		317.3 Volts RMS	Line overvoltage based on the actual L pin resistor used.
95	RDC_THEORETICAL		2.84 Ohms	Theoretical DS pin sense resistor.
96	RDC		2.87 Ohms	Standard (E96 / 1%) DS pin sense resistor.
97	CDC		10.0 u-Farads	Standard capacitor connected in parallel with the DS pin sense resistor.
98	VBIAS_MEASURED		12.0 Volts DC	Actual bias voltage (across the bias capacitor) measured on the bench.
99	VO_MEASURED		75.0 Volts DC	Actual load voltage measured on the bench.
100	ROC		100.0 k-Ohms	Standard (E96 / 1%) OC pin resistor.
101	IO_ACTUAL		160.0 m-Amperes	Actual output current seen on the bench.
102	RFB_THEORETICAL		41.8 k-Ohms	Calculated value of RFB, using standard values for RDS, ROVP, and RL
103	RFB		42.2 k-Ohms	Standard (E96 / 1%) F pin resistor.
104	CFB		150.0 n-Farads	Standard capacitor connected to the F pin.

Figure 13. Feedback and Protection Parameters with Fine Tuning of the Design Spreadsheet.

### Line-Sense Resistor, RL [E93]

Line-sense resistor is used for line compensation for regulation, phase angle measurement in dimming, line input overvoltage detection. To achieve accurate output current regulation and accurate line measurement a resistor with 1% tolerance is recommended. It is also recommended to use 2-1206 or 2-1/4 W package resistor for high-line application and 1-1206 or 1-1/4 W for low-line application.

$$R_L = VAC_{MAX} \times \sqrt{2} / I_{LOV}$$

### Line Overvoltage, OVP\_LINE [E94]

This protection is against line surge or swell. The unit will enter to auto restart when the threshold is reached. The spreadsheet will calculate the equivalent RMS input voltage for OVP.

$$OVP_{LINE} = R_L \times I_{LOV} \times \sqrt{2}$$

Where;

$I_{LOV}$ : Current threshold for input overvoltage at typical value of 120  $\mu$ A in the data sheet.

### Theoretical Drain Current Sense Resistor, RDC\_THEORETICAL [E95]

The ideal resistor value to be used in the drain current sensing is calculated. The voltage drop across the resistor is sensed through DS pin and the recommended average voltage drop across this sense resistor is 200 mV.

### Standard Drain Current Sense Resistor, RDC [E96]

This identifies standard 1% resistor value nearest to the RDC\_THEORETICAL to lessen the need of paralleling another resistor for centering the output, also saves cost and space (Figure 8).

### Capacitance Across Drain Current Sense Resistor, CDC [E97]

This is the capacitor (CDC) across the drain current sense resistor (RDC) that filters the switching drain current to reduce the IRMS power dissipation across the sense resistor.

### Actual Output Voltage, VO\_MEASURED [E99]

Enter the actual output voltage with LED load for fine tuning the output current.

### Output Current Compensation Resistor, ROC [E100]

Load variation, output overvoltage protection and output short-circuit is monitored through bias voltage via compensating resistor (ROC). Spreadsheet will calculate this resistance based from the actual bias voltage (VBIAS\_MEASURED). A 1% tolerance resistor is recommended in this location for tight output current tolerance.

### Actual Output Current, IO\_ACTUAL [E101]

Enter the actual current as measured from the bench for the fine tuning of external components to center the output to a desired level.

### Theoretical Feedback Resistor, RFB\_THEORETICAL [E102]

Spreadsheet calculates the exact feedback resistor resistance to set the output current based from the actual output current measured.

### Feedback Resistor, RFB [E103]

The spreadsheet will determine the nearest single resistance to use for RFB to avoid paralleling of components to get the desired current. But if the application requires tight output current tolerance then use the resistance calculated by RFB\_THEORETICAL.

### Feedback Filter Capacitance, CFB [E104]

Filter capacitance for the feedback current to average the signal to a desired voltage mean level of the FEEDBACK pin. The desired time constant is in the range of 3 ms to 6 ms to maintain stable operation with tight current regulation.

$$t_C = C_{FB} \times R_{FB}$$

PIXIs Design Spreadsheet for other topologies is available in PI public website (<https://piexpertonline.power.com/site/login>)

**Appendix A:**  
**LYTSwitch-5 Topology Configurations**

Basic Circuit Schematic	Key Features
<p style="text-align: right;">PI-7938-071916 Buck</p>	<p><b>Buck</b></p> <p><b>Benefits</b></p> <ul style="list-style-type: none"> <li>• Highest efficiency</li> <li>• Lowest component count – small size</li> <li>• Simple low-cost power inductor</li> <li>• Low drain source voltage stress</li> <li>• Best EMI/lowest component count for filter</li> </ul> <p><b>Limitations</b></p> <ul style="list-style-type: none"> <li>• Non-Isolated</li> </ul>
<p style="text-align: right;">PI-7939-071916 BB</p>	<p><b>Buck-Boost</b></p> <p><b>Benefits</b></p> <ul style="list-style-type: none"> <li>• Ideal for non-isolated high output voltage designs</li> <li>• High efficiency</li> <li>• Low component count</li> <li>• Simple common low-cost power inductor can be used</li> <li>• Lowest THD</li> </ul> <p><b>Limitations</b></p> <ul style="list-style-type: none"> <li>• Maximum VOUT is limited by MOSFET breakdown voltage</li> <li>• Non-isolated</li> </ul>
<p style="text-align: right;">PI-7942-071916 Boost</p>	<p><b>Boost</b></p> <p><b>Benefits</b></p> <ul style="list-style-type: none"> <li>• Ideal for non-isolated high output voltage designs; <math>V_o &gt; V_{in}</math></li> <li>• Highest efficiency</li> <li>• Lowest component count</li> <li>• Simple common low-cost power inductor</li> </ul> <p><b>Limitations</b></p> <ul style="list-style-type: none"> <li>• Maximum VOUT is limited by MOSFET breakdown voltage</li> <li>• Single input line voltage range</li> <li>• Non-isolated</li> <li>• High THD</li> </ul>

Figure 14. Buck Topology.

Figure 15. Buck-Boost Topology.

Figure 16. Boost Topology.

## Basic Circuit Schematic

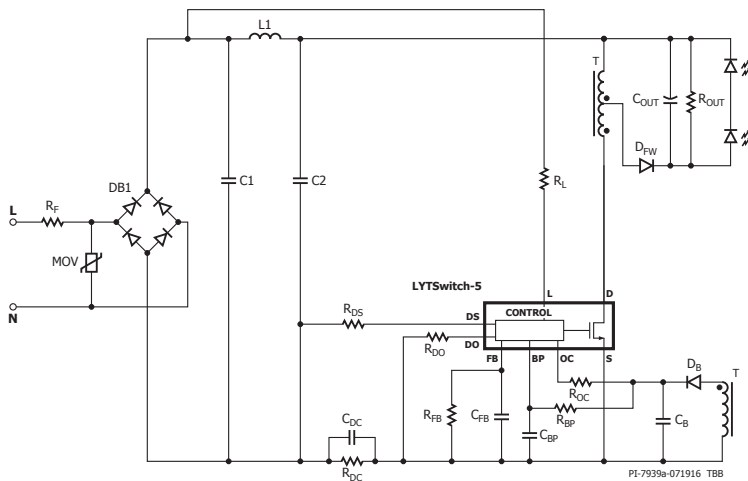


Figure 17. Tapped Buck-Boost Topology.

## Key Features

## Tapped Buck-Boost

## Benefits

- Ideal for low output voltage designs (<25 V)
- Simple common low-cost tapped inductor
- Low THD

## Limitations

- Maximum VOUT is limited by MOSFET breakdown voltage

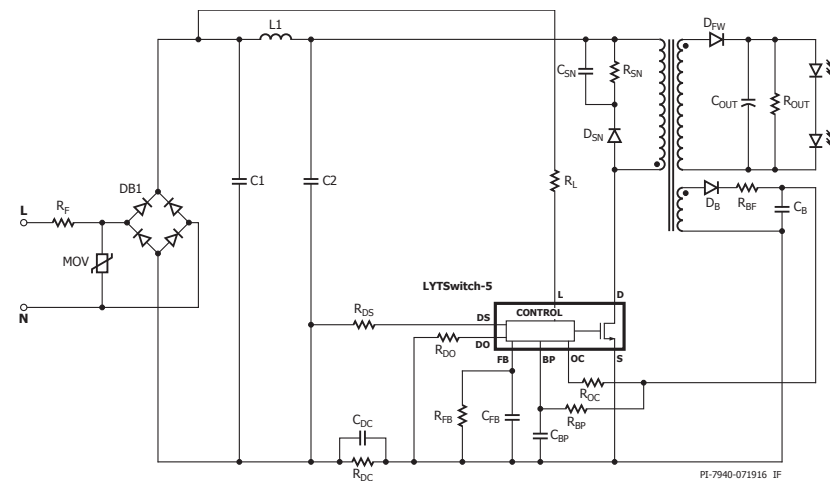


Figure 18. Isolated Flyback Topology.

## Isolated Flyback

## Benefits

- Provides isolated output
- Supports widest range of output voltages
- Lowest THD

## Limitations

- Flyback transformer
- Overall efficiency reduced by parasitic capacitance and inductance in the transformer
- Larger PCB area to meet isolation requirements
- Requires additional components (primary clamp and bias)
- Higher RMS switch and winding currents increases losses and lowers efficiency

 


Figure 19. Non-Isolated Flyback Topology.

## Non-Isolated Flyback

## Benefits

- Direct sensing of output current
- Supports widest range of output voltages
- Low THD

## Limitations

- Flyback transformer
- Overall efficiency reduced by parasitic capacitance and inductance in the transformer
- Larger PCB area to meet isolation requirements
- Requires additional components (primary clamp and bias)
- Higher RMS switch and winding currents increases losses and lowers efficiency

Revision	Notes	Date
A	Initial Release.	07/16

### For the latest updates, visit our website: [www.power.com](http://www.power.com)

Power Integrations reserves the right to make changes to its products at any time to improve reliability or manufacturability. Power Integrations does not assume any liability arising from the use of any device or circuit described herein. POWER INTEGRATIONS MAKES NO WARRANTY HEREIN AND SPECIFICALLY DISCLAIMS ALL WARRANTIES INCLUDING, WITHOUT LIMITATION, THE IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF THIRD PARTY RIGHTS.

### Patent Information

The products and applications illustrated herein (including transformer construction and circuits external to the products) may be covered by one or more U.S. and foreign patents, or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations patents may be found at [www.power.com](http://www.power.com). Power Integrations grants its customers a license under certain patent rights as set forth at <http://www.power.com/ip.htm>.

### Life Support Policy

POWER INTEGRATIONS PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF POWER INTEGRATIONS. As used herein:

1. A Life support device or system is one which, (i) is intended for surgical implant into the body, or (ii) supports or sustains life, and (iii) whose failure to perform, when properly used in accordance with instructions for use, can be reasonably expected to result in significant injury or death to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

The PI logo, TOPSwitch, TinySwitch, SENZero, SCALE-iDriver, Qspeed, PeakSwitch, LYTSwitch, LinkZero, LinkSwitch, InnoSwitch, HiperTFS, HiperPFS, HiperLCS, DPA-Switch, CAPZero, Clampless, EcoSmart, E-Shield, Filterfuse, FluxLink, StakFET, PI Expert and PI FACTS are trademarks of Power Integrations, Inc. Other trademarks are property of their respective companies. ©2016, Power Integrations, Inc.

## Power Integrations Worldwide Sales Support Locations

### World Headquarters

5245 Hellyer Avenue  
San Jose, CA 95138, USA.  
Main: +1-408-414-9200  
Customer Service:  
Phone: +1-408-414-9665  
Fax: +1-408-414-9765  
e-mail: [usasales@power.com](mailto:usasales@power.com)

### China (Shanghai)

Rm 2410, Charity Plaza, No. 88  
North Caoxi Road  
Shanghai, PRC 200030  
Phone: +86-21-6354-6323  
Fax: +86-21-6354-6325  
e-mail: [chinasales@power.com](mailto:chinasales@power.com)

### China (Shenzhen)

17/F, Hivac Building, No. 2, Keji Nan  
8th Road, Nanshan District,  
Shenzhen, China, 518057  
Phone: +86-755-8672-8689  
Fax: +86-755-8672-8690  
e-mail: [chinasales@power.com](mailto:chinasales@power.com)

### Germany

Lindwurmstrasse 114  
80337 Munich  
Germany  
Phone: +49-895-527-39110  
Fax: +49-895-527-39200  
e-mail: [eurosales@power.com](mailto:eurosales@power.com)

### Germany

HellwegForum 1  
59469 Ense  
Germany  
Tel: +49-2938-64-39990  
e-mail: [igbt-driver.sales@power.com](mailto:igbt-driver.sales@power.com)

### India

#1, 14th Main Road  
Vasanthanagar  
Bangalore-560052 India  
Phone: +91-80-4113-8020  
Fax: +91-80-4113-8023  
e-mail: [indiasales@power.com](mailto:indiasales@power.com)

### Italy

Via Milanese 20, 3rd. Fl.  
20099 Sesto San Giovanni (MI) Italy  
Phone: +39-024-550-8701  
Fax: +39-028-928-6009  
e-mail: [eurosales@power.com](mailto:eurosales@power.com)

### Japan

Kosei Dai-3 Bldg.  
2-12-11, Shin-Yokohama,  
Kohoku-ku  
Yokohama-shi, Kanagawa  
222-0033 Japan  
Phone: +81-45-471-1021  
Fax: +81-45-471-3717  
e-mail: [japansales@power.com](mailto:japansales@power.com)

### Korea

RM 602, 6FL  
Korea City Air Terminal B/D, 159-6  
Samsung-Dong, Kangnam-Gu,  
Seoul, 135-728, Korea  
Phone: +82-2-2016-6610  
Fax: +82-2-2016-6630  
e-mail: [koreasales@power.com](mailto:koreasales@power.com)

### Singapore

51 Newton Road  
#19-01/05 Goldhill Plaza  
Singapore, 308900  
Phone: +65-6358-2160  
Fax: +65-6358-2015  
e-mail: [singaporesales@power.com](mailto:singaporesales@power.com)

### Taiwan

5F, No. 318, Nei Hu Rd., Sec. 1  
Nei Hu Dist.  
Taipei 11493, Taiwan R.O.C.  
Phone: +886-2-2659-4570  
Fax: +886-2-2659-4550  
e-mail: [taiwansales@power.com](mailto:taiwansales@power.com)

### UK

Cambridge Semiconductor,  
a Power Integrations company  
Westbrook Centre, Block 5, 2nd Floor  
Milton Road  
Cambridge CB4 1YG  
Phone: +44 (0) 1223-446483  
e-mail: [eurosales@power.com](mailto:eurosales@power.com)